

## Lab 2 Practice

### Prerequisites

Concept	Video Lectures	in this lab
Data flow modeling	CT Verilog series 04	Wire, reg, signed, etc
Behavioral modeling	CT Verilog series 05 ~ 06	Always block
Sequential blocks	CT Verilog series 07	Synchronous output with clock

It is strongly recommended that you complete these practice exercises to prepare for the basic lab.

### 1. Summation with 1-Cycle Delay (40%)

Design a simple circuit that outputs the sum of two signed 8-bit inputs (A, B).

1. To prevent potential timing issues, the sum must be stored in a **flip-flop (FF)** before being sent to the output, introducing a **1-cycle delay**.
2. The output is updated at the **positive edge of the clock**.
3. The reset is **synchronous, active-high**. When reset is asserted, the output should be **0**.
4. Complete the Verilog template lab2\_1\_practice.v with the provided testbench and pattern file (lab2\_1\_practice\_t.v, pattern\_A\_practice.dat). Refer to the Appendix for instructions on adding the pattern files to simulation sources.
5. Your design must pass simulation, which will display the following PASS message:

```
scores = 40 / 40  
  
PASS!
```

**IO List and Specification:**

Signal	I/O	Bit Width	Description
clk	input	1	Clock (positive-edge triggered)
rst	input	1	Synchronous active-high reset
A	input	8	Signed operand
B	input	8	Signed operand
out	output	12	Signed result: A+B (delayed by 1 cycle)


The sum must appear **1 cycle after inputs are given**.

**Example**

Cycle	A	B	out (after 1 cycle)
1	-8'd1	8'd3	x
2	8'd2	-8'd2	12'd2
3	-8'd2	-8'd2	12'd0
4	8'd127	8'd127	-12'd4
5	-8'd1	-8'd1	12'd254

x indicates “don’t care”.

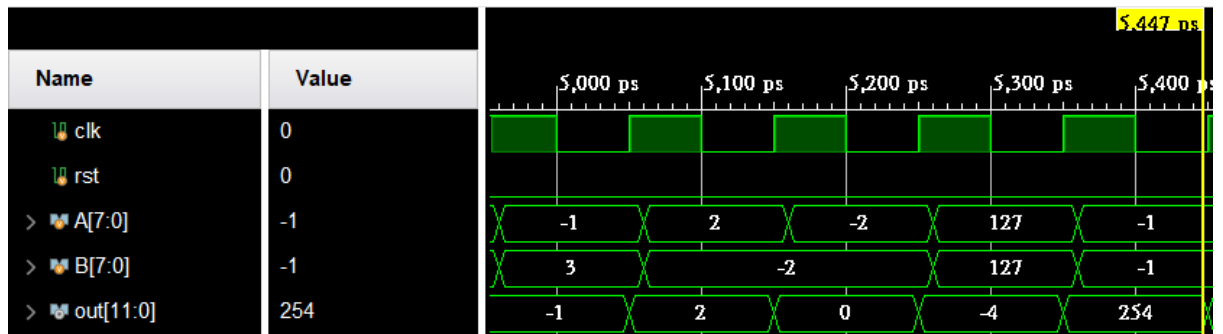Refer to the following waveform for a correct output example:



The radix of **A** , **B** and **out** is signed decimal on the waveform.

## Notes

- **Do not modify** the testbench or patterns.
- The TA will use the same testbench with additional hidden patterns to test your design for the basic lab. The grading is based on correctness. Pass/Fail messages of the testbench are only to assist the debugging.
- Ensure your design correctly handles **signed arithmetic**.

## 2. Subtraction with 2-Cycle Delay (60%)

Design a circuit that computes the subtraction of two signed 8-bit inputs (A, B).

1. The result must appear at the output **2 clock cycles** after the inputs are given.
2. The output is updated at the positive edge of the clock.
3. The reset is synchronous, active-high. When reset is asserted, the output should be 0.
4. Complete the Verilog template lab2\_2\_practice.v with the provided testbench and pattern files (lab2\_2\_practice\_t.v, pattern\_B\_practice.dat). Refer to the Appendix for instructions on adding the pattern files to simulation sources.
5. Your design must pass simulation, which will display the following PASS message:

```
scores = 60 / 60
```

```
PASS!
```

### IO List and Specification:

Signal	I/O	Bit Width	Description
clk	input	1	Clock (positive-edge triggered)
rst	input	1	Synchronous active-high reset
A	input	8	Signed operand
B	input	8	Signed operand
out	output	12	Signed result: A-B (delayed by 2 cycles)


The subtraction must appear **2 cycles after inputs are given**.

## Example

Cycle	A	B	out(after 2 cycle)
1	-8'd75	8'd22	x
2	8'd35	-8'd76	x
3	-8'd18	8'd16	-12'd97
4	-8'd69	-8'd11	12'd111
5	-8'd19	-8'd19	-12'd34

x indicates “don’t care”.

 Refer to the following waveform for a correct output example:



The radix of **A** , **B** and **out** is signed decimal on the waveform.

## Notes

- **Do not modify** the testbench or patterns.
- The TA will use the same testbench with additional hidden patterns to test your design for the basic lab. The grading is based on correctness. Pass/Fail messages of the testbench are only to assist the debugging.
- Ensure your design correctly handles **signed arithmetic**.

## Appendix: Adding Pattern Files to Vivado Simulation

