

Lab 2 Basic

1. Sign Bit Detector with 1-Cycle Delay (40%)

Design a simple circuit that checks the sign of two signed 8-bit inputs (A, B) and outputs a **2-bit code** based on their signs.

1. To prevent potential timing issues, the output must be stored in a **flip-flop (FF)**, introducing a **1-cycle delay**.
2. The output is updated at the **positive edge of the clock**.
3. The reset is **synchronous, active-high**. When reset is asserted, the output should be **0**.
4. Complete the Verilog template lab2_1.v with the provided testbench and pattern file (lab2_1_t.v, pattern_A.dat).
Refer to the Appendix for instructions on adding the pattern files to simulation sources.
5. Your design must pass simulation, which will display the following PASS message:

```
Both positive : 7 / 7
Both negative : 7 / 7
Different signs : 14 / 14
At least one is zero : 12 / 12
scores = 40 / 40
PASS!
```

IO List and Specification:

Signal	I/O	Bit Width	Description
clk	input	1	Clock (positive-edge triggered)
rst	input	1	Synchronous active-high reset
A	input	8	Signed input
B	input	8	Signed input
out	output	2	Encoded output

Input (A , B)	Output Code
Both positive	2'b01
Both negative	2'b10
Different signs	2'b11
At least one is zero	2'b00


The output must appear **1 cycle after inputs are given**.

Example

Cycle	A	B	out (after 1 cycle)
1	8'd0	8'd0	x
2	8'd127	8'd126	2'b00
3	-8'd128	-8'd128	2'b01
4	8'd1	-8'd128	2'b10
5	-8'd128	8'd1	2'b11

x indicates “don’t care”.

 Refer to the following waveform for a correct output example:



The radix of **A** and **B** is signed decimal; the radix of **out** is binary.

Grading:

Name	Score
Both positive	7%
Both negative	7%
Different signs	14%
At least one is zero	12%

Notes

- **Do not modify** the testbench or patterns.
- The TA will use the same testbench with additional hidden patterns to test your design for the basic lab. The grading is based on correctness. Pass/Fail messages of the testbench are only to assist the debugging.
- Pay attention to **signed number handling**.

2. Impulse-Triggered Arithmetic with Multi-Cycle Delay (60%)

Design a circuit that captures two signed 8-bit inputs (A, B) when impulse is asserted (i.e., `impulse == 1`), and produces two results with different delays.

1. The output is updated at the **positive edge of the clock**.
2. The reset is **synchronous, active-high**. When reset is asserted, the output should be **0**.
3. Complete the Verilog template `lab2_2.v` with the given testbench and pattern files (`lab2_2_t.v`, `pattern_B.dat`).
Refer to the Appendix for instructions on adding the pattern files to simulation sources.
4. Your design must pass simulation, which will display the following PASS message:

```
OUT1 : 30 / 30
OUT2 : 30 / 30
scores = 60 / 60
PASS!
```

IO List and Specification:

Signal	I/O	Bit Width	Description
clk	input	1	Clock (positive-edge triggered)
rst	input	1	Synchronous active-high reset
impulse	input	1	Triggers a calculation
A	input	8	Signed operand (2's complement)
B	input	8	Signed operand (2's complement)
OUT1	output	16	Concatenation of A and B
OUT2	output	8	$(\text{ABS}(A * B)) \% 128$

Once impulse is 1, the circuit captures A and B and performs the following operations:

Timing	Operation Description
After 1 cycle	OUT1 = Concatenation of A and B
After 3 cycles	OUT2= (ABS(A * B)) % 128

Each trigger (impulse==1) starts a new calculation.


- On every positive edge of clk, when impulse == 1, store the current values of A and B.
- After 1 clock cycle, output OUT1 = Concatenation of A and B
at all other cycles, OUT1 = 0.
- After 3 clock cycles, output OUT2 = (ABS(A * B)) % 128;
at all other cycles, OUT2 = 0.
- If rst == 1, both OUT1 and OUT2 are synchronously reset to 0.
- All operations use signed (2's complement) values.

Example

Cycle	impulse	A	B	OUT1 (after 1 cycle)	OUT2 (after 3 cycles)
1	1	-8'd121	8'd28	x	x
2	0	-8'd40	-8'd110	16'h871c	x
3	1	8'd118	-8'd126	16'h0000	x
4	0	-8'd55	-8'd124	16'h7682	8'd60
5	1	8'd25	8'd101	16'h0000	8'd0
6	1	8'd105	8'd73	16'h1965	8'd20

x indicates “don’t care”.

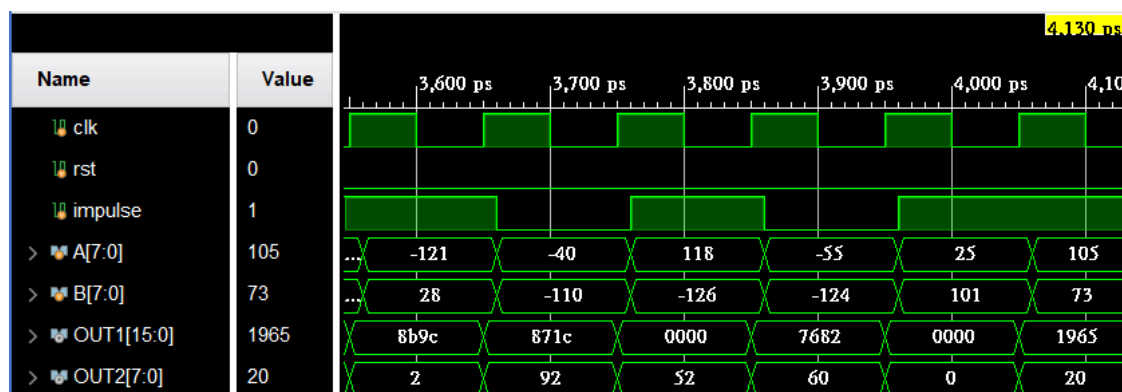Refer to the following waveform for a correct output example:



The radix of **A** , **B** and **OUT2** is signed decimal; the radix of **OUT1** is

hexadecimal.

Grading:

Name	Score
OUT1	30%
OUT2	30%

Notes

- **Do not modify** the testbench or patterns.
- The TA will use the same testbench with additional hidden patterns to test your design for the basic lab. The grading is based on correctness. Pass/Fail messages of the testbench are only to assist the debugging.
- Ensure proper **signed arithmetic handling** and timing.

Appendix: Adding Pattern Files to Vivado Simulation

