

## Lab 2 Advanced: FPGA Implementation of 3-SAT Solving

### Submission Due Dates:

Demo:	2025/09/23 17:20
Source Code:	2025/09/23 18:30
Report:	2025/09/28 23:59

### Objectives

- Getting familiar with Verilog combinational/sequential behavior modeling.
- Practicing switch and LED control on the FPGA board.

### Introduction to the SAT problem

- $\vee$  (OR),  $\wedge$  (AND),  $\neg$  (NOT) are the Boolean operators.
- **Literal:** A literal is either a Boolean variable (e.g., A) or its negation (e.g.,  $\neg A$ ). For example, in the expression  $(A \vee \neg B)$ , both A and  $\neg B$  are literals.
- **Clause:** A clause is a disjunction (logical OR, denoted  $\vee$ ) of one or more literals. For example,  $(A \vee \neg B \vee C)$  is a clause with three literals.
- **SAT Problem:** Given a Boolean formula (a conjunction of clauses) and determine whether there exists an assignment of true/false values to its variables that makes the entire formula true. If such an assignment exists, the formula is said to be **satisfiable**.
- **3-SAT problem** is that there are exactly 3 literals in each clause.

Examples for 3-SAT problem:

1. Satisfiable:

$$(A \vee B \vee \neg C) \wedge (\neg A \vee B \vee D) \wedge (\neg C \vee \neg D \vee E)$$

clause1          clause2          clause3

In this example, one satisfying assignment: A=1, B=0, C=1, D=1, E=1.

2. Unsatisfiable:

$$(A \vee A \vee A) \wedge (\neg A \vee \neg A \vee \neg A)$$

clause1          clause2

In this example, no assignment for A can satisfy both clauses.

For more details, see Wikipedia: Boolean Satisfiability Problem:


[https://en.wikipedia.org/wiki/Boolean\\_satisfiability\\_problem](https://en.wikipedia.org/wiki/Boolean_satisfiability_problem)

## Action Items
 
### 1. lab2\_adv\_1.v (35%)

Design a circuit that solves a 3-SAT problem with 4 clauses using brute force.

- Try all  $2^3$  possibilities (from 3'b000 to 3'b111) in one cycle to determine if the formula is satisfiable
- Output the first satisfying Boolean assignment, if it exists.



#### a. IO List and Specification


Input Signals	Bit Width
clk	1
rst	1
clause_1	9
clause_2	9
clause_3	9
clause_4	9

Output Signals	Bit Width
out	3
satisfaction	1

- clk:
  - A 100 MHz clock.
  - All outputs should change at positive edges.
- rst:
  - **Synchronous active-high reset**; when rst == 1'b1, reset all outputs to 0
- clause\_1, clause\_2, clause\_3, clause\_4:
  - There are 3 variables (A, B, and C), encoded by 2'b00, 2'b01, 2'b10, respectively. We use one additional bit to indicate whether the variable is negated. Therefore, each literal is represented using 3 bits: the leftmost bit indicates negation, and the two rightmost bits represent the variable ID (00→A, 01→B, 10→C).


For example, 3'b010 corresponds to C, 3'b101 corresponds to  $\neg B$ .

 - Each clause contains three literals. Therefore, we use 9 bits to represent a clause. For example, the clause 9'b100\_001\_010 corresponds to  $\neg A \vee B \vee C$ .



- Note that clauses may update at the negative clock edge.
- out:
  - You need to test the Boolean assignment from 3'b000 to 3'b111, when the design finds the **first** Boolean assignment for the variables that satisfies the entire Boolean formula ( $\text{clause\_1} \wedge \text{clause\_2} \wedge \text{clause\_3} \wedge \text{clause\_4}$ ), the **out** signal indicates the 3-bit assignment.
  - The variable A, denoted by 2'b00, corresponds to out[0]. The variable B, denoted by 2'b01, corresponds to out[1]. The variable C denotes by 2'b10 corresponds to out[2]. (e.g., 3'b100 for C=1, B=0, A=0; 0 for false and 1 for True).
  - Otherwise, **out** should be 3'b111.
  - The **out** signal updates at the **positive clock edge**.
- satisfaction:
  - When the FPGA finds a satisfying assignment, satisfaction is set to 1'b1.
  - Otherwise, it remains 1'b0.
  - The **satisfaction** signal updates at the **positive clock edge**.
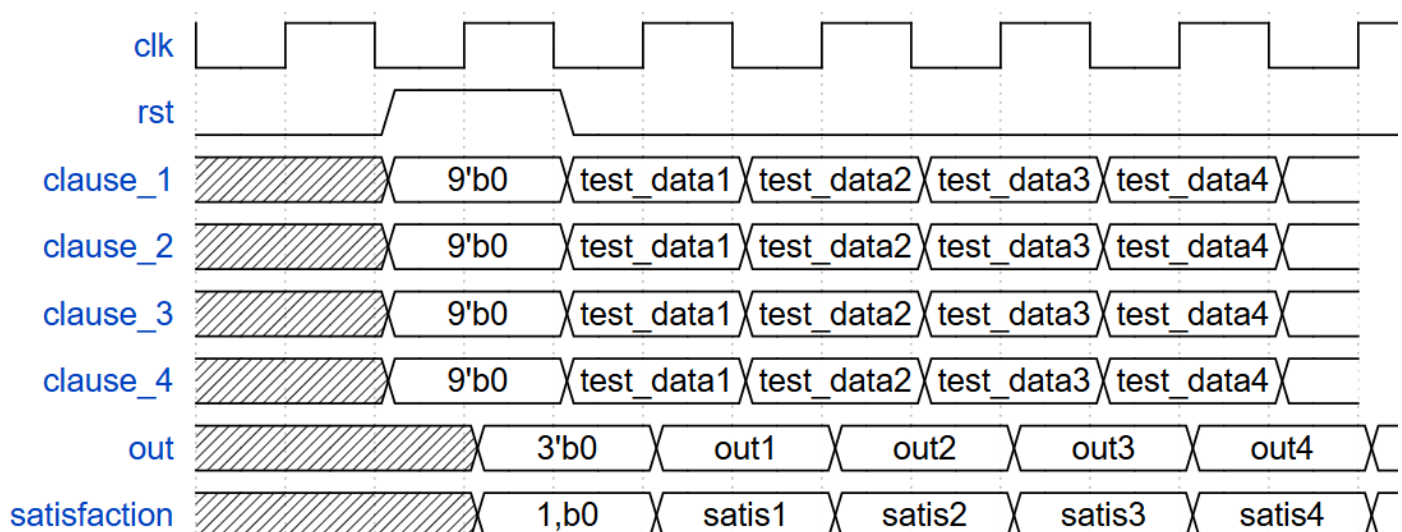
## b. Waveform example for the input/output



- After rst goes low, the test begins, and input data (clauses) are updated at the **negative clock edge**.
- Use the brute-force method to evaluate the formula by testing all possible Boolean assignments within one cycle.
  - Evaluate the Boolean assignment from 3'b000, 3'b001, 3'b010, to 3'b111.
- After the negative edge (when inputs are updated), update the outputs (out and satisfaction) at the next positive clock edge.
- Therefore, the circuit produces a new result every cycle, and each output value remains valid for exactly one cycle.

**c. You must use the following template for your design**

```
`timescale 1ns/1ps
module lab2_adv_1 (
    input clk,
    input rst,
    input [8:0] clause_1,
    input [8:0] clause_2,
    input [8:0] clause_3,
    input [8:0] clause_4,
    output reg satisfaction,
    output [2:0] out
);


    // Output signals can be reg or wire
    // add your design here

endmodule
```
 
## 2. lab2\_adv\_1\_t.v (15%)

Write your own testbench (lab2\_adv\_1\_t.v) to verify the design (lab2\_adv\_1.v). In your report, please explain how you built your testbench.

The testbench must at least cover the patterns as in the following waveform:



Brief summary of the testbench (refer to the waveform above):

- The duration of the simulation is 120ns.
- The reset signal (rst) must be activated at 15ns and last for 20 ns.
- Test data: 8 sets of clause inputs (provided in the template).
- The evaluation starts at 35ns (when rst goes down).

- The inputs ('clause\_1', 'clause\_2', 'clause\_3', and 'clause\_4') change at **negative clock edges**.
- The outputs ('out' and 'satisfaction') change their values at **positive clock edges**.


### 3. lab2\_adv\_2.v (50%)

Implement a 3-SAT verification system on the FPGA.

- Inputs:** Three clauses and a Boolean assignment entered via the switches.
- Outputs:** Satisfaction result displayed by the LEDs.

#### a. IO List and Specification

Input Connection	
rst	Connected to SW15
valid	Connected to SW14
switch_inputtype	Connected to SW13-SW12
switch_input	Connected to SW8-SW0
Output Connection	
out	Connected to LD13-LD0
satisfaction	Connected to LD15

 

- rst
  - Asynchronous active-high reset**; when rst == 1'b1, reset outputs to 0.
- valid
  - If valid == 1'b1, load switch inputs into the design.
  - If valid == 1'b0, no matter how the switches are changed, the values of the clauses and Boolean assignment remain unchanged.
- switch\_inputtype
  - Determines which clause is updated by the value of switch\_input:
    - 2'b00 and valid==1: load clause\_1 (9-bit value from SW8-SW0).

- b. 2'b01 and valid==1: load clause\_2 (9-bit value from SW8-SW0).
  - c. 2'b10 and valid==1: load clause\_3 (9-bit value from SW8-SW0).
  - d. 2'b11 and valid==1: load the Boolean assignment (3-bit value from SW2-SW0; SW8-SW3 unused).
- Once the value of switch\_inputtype changed, the previous input should be stored if valid==1'b1.
- switch\_input
  - Clause input (9 bits: SW8-SW0):  
Where SW8 is the most significant bit and SW0 is the least significant bit. For example: 9'b000\_101\_010 (SW8, SW7..., SW1, SW0)
  - Boolean assignment (3 bits: SW2-SW0):
    - a. Variable A → SW0
    - b. Variable B → SW1
    - c. Variable C → SW2
 For example, if SW0 is on (SW0=1), A=1.
  - Each clause has an initial value of 9'b000\_000\_000; The Boolean assignment has an initial value of 3'b000.
- satisfaction
  - LD15 is set to 1'b1 if all three clauses are satisfied.
  - Otherwise, LD15 is set to 1'b0.
- out: (per-clause satisfaction)
  - If Clause 1 is satisfied, LD13-LD10 = 4'b1111.
  - If Clause 2 is satisfied, LD8-LD5 = 4'b1111.
  - If Clause 3 is satisfied, LD3-LD0 = 4'b1111.
  - LD9 and LD4 remain 1'b0.

## b. Example Operations

Step	Action	Register Values	out	satisfaction
1	SW15=1	Clause1: 000_000_000 Clause2: 000_000_000 Clause3: 000_000_000 Boolean Assignment (BA): 000	0000000000000000	0
2	SW15=0	Clause1: 000_000_000 Clause2: 000_000_000 Clause3: 000_000_000 Boolean Assignment (BA): 000	0000000000000000	0
3	SW14=1 SW2=1 (Clause 1)	Clause1: 000_000_100 Clause2: 000_000_000 Clause3: 000_000_000 BA: 000	1111000000000000	0
4	SW14=0 SW2=0 SW12=1 SW5=1 SW14=1 (Clause 2)	Clause1: 000_000_100 Clause2: 000_100_000 Clause3: 000_000_000 BA: 000	1111011110000000	0
5	SW14=0	Clause1: 000_000_100	11110111101111	1

	SW5=0 SW12=0 SW13=1 SW8=1 SW14=1 (Clause 3)	Clause2: 000_100_000 Clause3: 100_000_000 BA: 000		
6	SW14=0 SW8=0 SW12=1 SW0=1 SW14=1 (Boolean Assignment)	Clause1: 000_000_100 Clause2: 000_100_000 Clause3: 100_000_000 BA: 001	11110111101111	1
7	SW14=0 SW0=0 SW13=0 SW2=1 SW5=1 SW8=1 SW14=1 (Clause 2)	Clause1: 000_000_100 Clause2: 100_100_000 Clause3: 100_000_000 BA: 001	11110000001111	0

- **Steps 1 and 2:**
  - a. Reset the value of clauses, Boolean assignment, and output signals to 0.
- **Step 3:**
  - a. Set SW14 (valid bit) to 1. Now the value of SW8-SW0 corresponds to Clause 1 (switch\_inputtype=2'b00).
  - b. Then set SW2 to change the value of Clause 1.
  - c. Since the Boolean assignment (3'b000) satisfies Clause 1, LD13-LD10 is 4'b1111.
- **Step 4:**
  - a. Set SW14 (valid) to 0. Then set SW2=0.
  - b. Set SW12=1. Now switch\_inputtype=2'b01 (Clause 2).
  - c. Set SW5=1 and SW14=1 to change the value of Clause 2.
  - d. Since the Boolean assignment (3'b000) satisfies Clause 2, LD8-LD5 is 4'b1111.
- **Step 5:**
  - a. Set SW14=0 and then SW5=0.
  - b. Set SW12=0 and SW13=1 (switch\_inputtype=2'b10: Clause 3).
  - c. Set SW8=1 and then SW14=1 to change the value of Clause 3.
  - d. Since the Boolean assignment (3'b000) satisfies Clause 3, LD3-LD0 is 4'b1111.  
Moreover, because all the 3 clauses are satisfied, the satisfaction bit becomes 1.
- **Step 6:**
  - a. Set SW14=0 and then SW8=0.
  - b. Set SW12=1 (switch\_inputtype=2'b11: Boolean assignment).
  - c. Set SW0=1 and then SW14=1 to change the Boolean assignment to 3'b001.  
Although we have changed the Boolean assignment, the assignment still satisfies all 3 clauses. Therefore, the satisfaction is still 1, and the out signal is still 14'b11110111101111.
- **Step 7:**

- a. Set SW14=0 and then SW0=0.
- b. Set SW13=0 (switch\_inputtype=2'b01: Clause 2).
- c. Set SW2=SW5=SW8=1 and then SW14=1 to change the value of Clause 2.
- d. Since the Boolean assignment (3'b001) doesn't satisfy Clause 2, LD8-LD5 is 4'b0000.

**c. You must use the following template for your design**

```
module lab2_adv_2 (  
    input clk,  
    input rst,  
    input [8:0] switch_input,  
    input [1:0] switch_inputtype,  
    input valid,  
    output reg [13:0] out,  
    output reg satisfaction  
);  
// Output signals can be reg or wire  
// add your design here  
  
endmodule
```

## 4. Questions & Discussion

Please answer the following questions in your report.

1. What are the differences between a combinational circuit and a sequential circuit? Please explain how each of them works in detail.
2. For an **unsatisfiable 3-SAT problem**, how would you extend your Verilog design to solve the **MAX-SAT** problem (find a Boolean assignment that satisfies the maximum number of clauses)?
3. In lab2\_adv\_2, what **unexpected behavior** might occur if the valid signal is removed? Explain why?

## 5. Report Guidelines

Your report should include but not limit to the following items.

- A. Lab Implementation (35%)
  1. Block diagram of the design with explanation.
  2. Description of each essential block.
  3. State diagram(s) for FSM(s) with explanation, if applicable.
  4. Waveform screenshots and testing process, with explanation.
- B. Questions & Discussions (50%)

Provide your answer to the Questions & Discussions in the lab assignment.
- C. Problem Encountered (10%)

Describe the problems you encountered, solutions you developed, and the discussion. Explaining them with code segments or diagrams is recommended.
- D. Suggestions (5%)

Optional: Feedback on the lab, course suggestions, or even a light-hearted joke.



## Attention

- ✓ **DO NOT** copy-and-paste code segments from the PDF materials to compose your design. It may also paste invisible non-ASCII characters, leading to hard-to-debug syntax errors.
- ✓ You should hand in **three** source files, including **lab2\_adv\_1.v**, **lab2\_adv\_1\_t.v**, **lab2\_adv\_2.v**. **Upload each source file individually. DO NOT hand in any compressed ZIP files, which will be considered an incorrect format.**
- ✓ You should also hand in your report as **lab2\_adv\_report\_StudentID.pdf** (i.e., lab2\_adv\_report\_111456789.pdf).
- ✓ You should be able to answer questions from TA during the demo.
- ✓ You need to prepare the bitstream files before the lab demo to make the demo process smooth.